


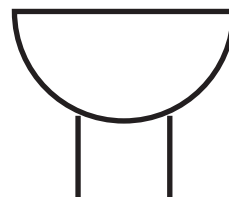
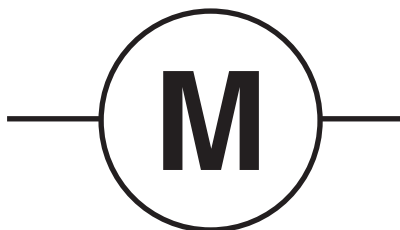


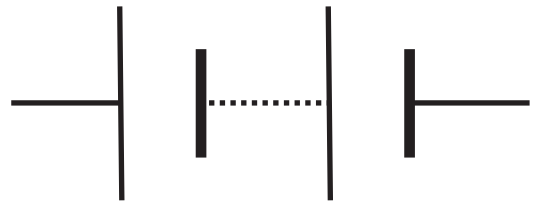

Circuit symbols

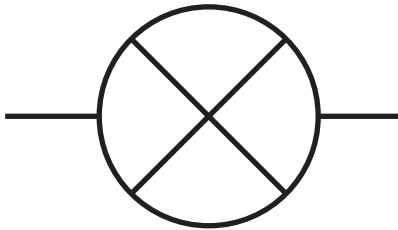

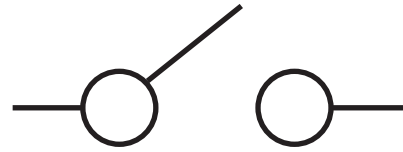

Circuit diagrams

Describe the components of the circuits, whether the bulb will light and why.

